

Second Edition

John G. Kassakian
David J. Perreault
George C. Verghese
Martin F. Schlecht



Principles of Power Electronics



Principles of Power Electronics

SECOND EDITION

John G. Kassakian

Massachusetts Institute of Technology

David J. Perreault

Massachusetts Institute of Technology

George C. Verghese

Massachusetts Institute of Technology

Martin F. Schlecht

SynQor Inc.

جامعة أمحمد بوقرة - بومرداس
Université M'hamed Bougara - Boumerdes
المكتبة الجامعية
رقم الجرد: 0144575

جامعة أمحمد بوقرة - بومرداس
Université M'hamed Bougara - Boumerdes
المكتبة الجامعية
621.317.381KAS
1exp.



CAMBRIDGE
UNIVERSITY PRESS

Contents

Preface	page xv
Acknowledgments	xviii
1 Introduction	1
1.1 Power Electronic Circuits	1
1.2 Power Semiconductor Switches	2
1.3 Transformers	5
1.4 Nomenclature	7
1.5 Bibliographies	8
1.6 Problems	8
Part I Form and Function	
2 Form and Function: An Overview	11
2.1 Functions of a Power Circuit	11
2.2 AC/DC Converters	13
2.3 DC/DC Converters	18
2.4 AC/AC Converters	20
2.5 Influence of Switch Implementation	22
Problems	24
3 Introduction to Rectifiers	27
3.1 Power in Electrical Networks	27
3.2 Single-Phase Half-Wave Rectifier	29
3.3 AC-Side Reactance and Current Commutation	35
3.4 Measures and Effects of Distortion	38
3.5 Bridge Rectifiers	44
Notes and Bibliography	49
Problems	50
4 Phase-Controlled Converters	57
4.1 Single-Phase Configurations	58
4.2 Phase Control with AC-Side Reactance	64
4.3 Inversion Limits	67

Notes and Bibliography	71
Problems	72
5 Pulse-Width-Modulated DC/DC Converters	76
5.1 The DC/DC Converter Topology	77
5.2 The Canonical Switching Cell	82
5.3 Direct Converter	82
5.4 Indirect Converter	89
5.5 Other PWM DC/DC Converters	92
5.6 Choice of Capacitor and Inductor Values	95
5.7 Semiconductor Device Stresses	103
5.8 Three-Level Flying-Capacitor Converter	104
5.9 Converter Operation with Discontinuous Conduction	106
Notes and Bibliography	108
Problems	109
6 Switched-Capacitor and Related Converters	116
6.1 Switched-Capacitor DC/DC Converter	116
6.2 Two-State Switched-Capacitor Converter	118
6.3 Switch Implementation	121
6.4 Other Switched-Capacitor DC/DC Converters	123
6.5 Other Kinds of Switched-Capacitor Converters	131
Notes and Bibliography	132
Problems	133
7 Isolated Pulse-Width-Modulated DC/DC Converters	136
7.1 Single-Ended Isolated Forward Converter	136
7.2 Double-Ended Isolated Forward Converter	145
7.3 Dual Active-Bridge Converter	150
7.4 Flyback Converter	153
7.5 Other PWM Isolated Converters	154
7.6 Effects of Transformer Leakage Inductance	155
7.7 Converters with Multiple Outputs	158
Notes and Bibliography	158
Problems	159
8 Single-Phase Switched-Mode DC/AC Converters	167
8.1 Basic Variable-Frequency Bridge Converter	167
8.2 Harmonic Reduction	172
8.3 Pulse-Width-Modulated DC/AC Converters	179
8.4 Current Control of Inverters	187

8.5	Multi-level Converters	190
8.6	Transformer-Isolated DC/AC Converters	192
8.7	Other DC/AC Converter Topologies	194
8.8	Power Balance in Single-Phase DC/AC Converters	196
8.9	Switched-Mode Rectifiers and Power Factor Correction	197
	Notes and Bibliography	202
	Problems	203
9	Polyphase Sources and Converters	207
9.1	Polyphase Sources	207
9.2	Three-Phase Sources	209
9.3	Introduction to Polyphase Rectifier Circuits	213
9.4	Phase-Controlled Three-Phase Converters	215
9.5	Commutation in Polyphase Rectifiers	216
9.6	Three-Phase Inverters	221
9.7	Space-Vector Representation and Modulation for Three-Phase Systems	229
9.8	Multi-Level Inverters	237
	Notes and Bibliography	242
	Problems	243
10	Resonant Converters	249
10.1	Review of Second-Order System Behavior	250
10.2	Quality Factor	254
10.3	Resonant Converter Analysis	256
10.4	Soft Switching of Resonant Converters	260
10.5	Resonant DC/DC Converters	264
10.6	Radio-Frequency Converters	271
	Notes and Bibliography	284
	Problems	285
11	AC/AC Converters	289
11.1	Introduction to AC/AC Converters	289
11.2	Energy Storage Requirements in a DC-Link Converter	290
11.3	The Naturally Commutated Cycloconverter	294
11.4	An Isolated High-Frequency-Link Cycloconverter	299
11.5	Solid-State Transformer	302
11.6	Matrix Converter	305
	Notes and Bibliography	306
	Problems	306

Part II Dynamic Models and Control

12 Dynamic Models and Control: An Overview	313
12.1 Dynamic Behavior of Power Converters	314
12.2 Dynamic Models	322
12.3 Averaged-Circuit Models	323
12.4 Linearized Models	329
12.5 Feedback Control	332
Notes and Bibliography	342
Problems	343
13 Averaged-Circuit and State-Space Models	346
13.1 Averaged-Circuit Models	346
13.2 Generalizing Circuit Averaging to the Fundamental Component	350
13.3 Continuous-Time State-Space Models	354
13.4 Discrete-Time or Sampled-Data Models	365
13.5 Generalized State-Space Models	368
13.6 Models for Controllers and Interconnected Systems	372
Notes and Bibliography	373
Problems	374
14 Linear Models and Feedback Control	378
14.1 Linearization	378
14.2 Linearizing an Averaged-Circuit Model	379
14.3 Linearizing Continuous-Time State-Space Models	383
14.4 Analysis of Continuous-Time LTI Models	385
14.5 Piecewise LTI Models	394
14.6 Linearizing Discrete-Time Generalized State-Space Models	395
14.7 Analysis of Discrete-Time LTI Models	399
14.8 Feedback Control Design	405
14.9 Multi-Loop Control	414
14.10 State Feedback	422
14.11 Digital Control	425
Notes and Bibliography	428
Problems	429
Part III Components and Devices	
15 Components and Devices: An Overview	437
15.1 Practical Semiconductor Switches	438
15.2 Practical Energy Storage Elements	438
15.3 Semiconductor Devices	439

15.4	Capacitors	452
15.5	Inductors and Transformers	455
	Problems	457
16	Review of Semiconductor Devices	461
16.1	Elementary Physics of Semiconductors	461
16.2	Simple Analysis of a Diode	472
16.3	Bipolar Junction Transistor	478
16.4	MOSFET	483
16.5	The Safe Operating Area	486
	Notes and Bibliography	487
	Problems	488
17	Power Semiconductor Devices	494
17.1	Bipolar Diode	494
17.2	Switch Transitions in a pin Diode	504
17.3	The Schottky Barrier Diode	507
17.4	Power BJT	511
17.5	Power MOSFET	517
17.6	Superjunction MOSFET	523
17.7	IGBT	524
17.8	Silicon Carbide and Gallium Nitride Devices	528
17.9	Thyristor	530
17.10	Datasheet	538
	Notes and Bibliography	541
	Problems	542
18	Introduction to Magnetism	545
18.1	Inductor	546
18.2	Saturation, Hysteresis, and Residual Flux	555
18.3	Losses In Magnetic Components	557
18.4	Transformers	566
18.5	Magnetic Material Properties	575
	Notes and Bibliography	576
	Problems	577
19	Magnetic Component Modeling	582
19.1	Mathematical Representation: Inductance Matrix	582
19.2	Circuit Representations for Two-Port Transformers	584
19.3	Determining Transformer Parameters	587
19.4	Multi-Winding Model	588

19.5	Extending the Magnetic Circuit Model Concept	597
19.6	Physical Electric Circuit Models for Magnetic Systems	603
	Notes and Bibliography	607
	Problems	608
20	Introduction to Magnetics Design	612
20.1	Filter Inductor Design and Core Factor	613
20.2	Thermal Constraints in Magnetics Design	618
20.3	Inductor Energy Storage Limits	621
20.4	AC Magnetics Sizing and Core Area Product	624
20.5	Performance Factor for Magnetic Materials	634
20.6	An Iterative Inductor Design Algorithm	636
	Notes and Bibliography	638
	Problems	640
21	Magnetics Loss Analysis and Design	643
21.1	Magnetic Diffusion	643
21.2	Winding Loss Calculation	655
21.3	Core Loss	675
	Notes and Bibliography	684
	Problems	686
Part IV	Practical Considerations	
22	Practical Considerations: An Overview	693
22.1	Gate and Base Drives	693
22.2	Thyristor Commutation Circuits	695
22.3	Snubbers, Clamps, and Soft Switching	697
22.4	Thermal Considerations	700
	Problems	701
23	Gate and Base Drives	704
23.1	MOSFET and IGBT Gate Drives	705
23.2	Bipolar Transistor Base Drives	713
23.3	Thyristor Gate Drives	716
	Notes and Bibliography	719
	Problems	719
24	Snubber Circuits, Clamps, and Soft Switching	724
24.1	Turn-Off Snubber	725
24.2	Turn-On Snubber	730

24.3 Combined Turn-On/Turn-Off Snubber	733
24.4 Alternative Placements of the Snubber Circuit	735
24.5 Dissipation in Snubber Circuits	736
24.6 Soft Switching	739
Notes and Bibliography	748
Problems	750
25 Thermal Modeling and Heat Sinking	753
25.1 Static Thermal Models	754
25.2 Thermal Interfaces	758
25.3 Transient Thermal Models	762
Notes and Bibliography	767
Problems	768
26 Electromagnetic Interference and Filtering	771
26.1 EMI Specifications and Measurement	771
26.2 Filter Design	773
26.3 Common-Mode and Differential-Mode Variables	781
26.4 Parasitics and Circuit Layout	787
Notes and Bibliography	789
Problems	790
Index	793