

This International Student Edition is for use outside of the U.S.

Electricity

Principles and Applications

NINTH EDITION

Mc
Graw
Hill


RICHARD J. FOWLER • MITCHEL E. SCHULTZ



Ninth Edition

Electricity

Principles & Applications

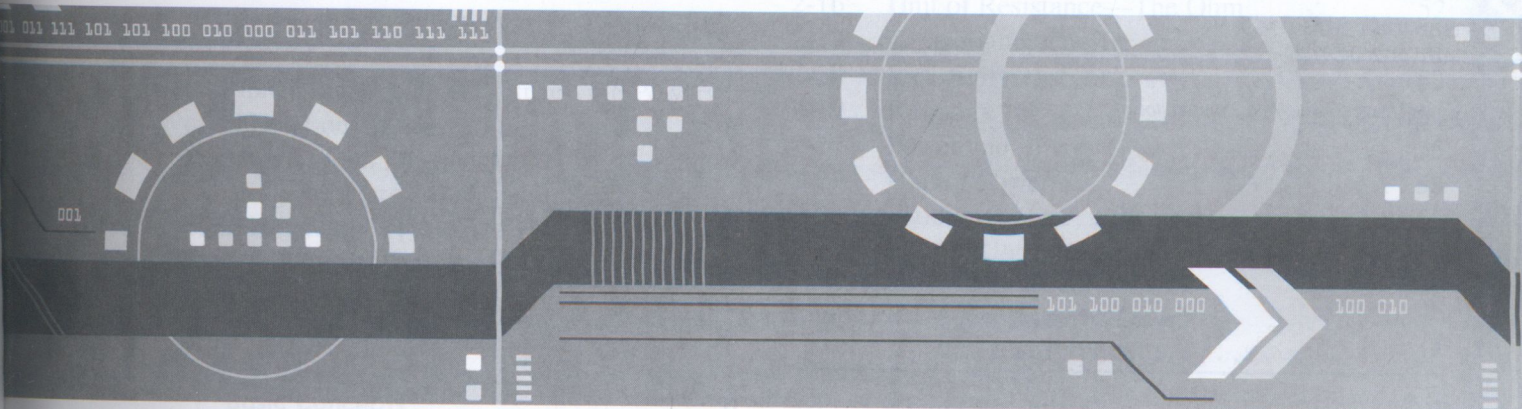

Richard J. Fowler
Mitchel E. Schultz

جامعة أمحمد بوقرة - بومرداس
Université M'hamed Bougara - Boumerdes
المكتبة الجامعية
رقم الجرد: 0.14.44.46

جامعة أمحمد بوقرة - بومرداس
Université M'hamed Bougara - Boumerdes
المكتبة الجامعية
رقم: 537.1/FOW

**Mc
Graw
Hill**

Contents

Preface	viii
Walkthrough.....	x
Acknowledgments	xiv
Safety	xv

Introduction I Introduction to Powers of 10 I

I-1 Scientific Notation	2
I-2 Engineering Notation and Metric Prefixes ...	4
I-3 Converting between Metric Prefixes.....	6
I-4 Addition and Subtraction Involving Powers of 10 Notation	7
I-5 Multiplication and Division Involving Powers of 10 Notation	8
I-6 Reciprocals with Powers of 10	9
I-7 Squaring Numbers Expressed in Powers of 10 Notation	9
I-8 Square Roots of Numbers Expressed in Powers of 10 Notation	10
I-9 The Scientific Calculator	10

Chapter I Basic Concepts 21

1-1 Work and Energy	21
1-2 Unit of Energy.....	22
1-3 Energy Conversion	23
1-4 Efficiency	24
1-5 Structure of Matter	26
1-6 Electric Charge	28
1-7 Valence Electrons	28
1-8 Free Electrons	29
1-9 Ions	29
1-10 Static Charge and Static Electricity	30
1-11 Static Discharge	31
1-12 Uses of Static Electricity	31

Chapter 2 Electrical Quantities and Units 41

2-1 Charge.....	41
2-2 Unit of Charge.....	41
2-3 Current and Current Carriers	42
2-4 Current in Solids.....	42
2-5 Current in Liquids and Gases	44
2-6 Current in a Vacuum.....	45

2-7 Unit of Current—The Ampere	46
2-8 Voltage	47
2-9 Unit of Voltage—The Volt	49
2-10 Polarity	50
2-11 Sources of Voltage	50
2-12 Resistance	52
2-13 Conductors	52
2-14 Insulators.....	52
2-15 Semiconductors.....	52
2-16 Unit of Resistance—The Ohm	52
2-17 Temperature Coefficient.....	53
2-18 Resistivity	53
2-19 Resistors	54
2-20 Power and Energy.....	55
2-21 Unit of Power	55
2-22 Efficiency	56
2-23 Special Units and Conversions	57

Chapter 3 Basic Circuits, Laws, and Measurements 67

3-1 Circuit Essentials	67
3-2 Circuit Symbols and Schematic Diagrams	68
3-3 Calculating Electrical Quantities	70
3-4 Measuring Electrical Quantities	76

Chapter 4 Circuit Components 89

4-1 Batteries and Cells	89
4-2 Lead-Acid Cells	91
4-3 Nickel-Cadmium Cells	95
4-4 Carbon-Zinc and Zinc Chloride Cells.....	96
4-5 Alkaline – Manganese Dioxide Cells.....	96
4-6 Mercuric Oxide Cells	97
4-7 Silver Oxide Cells.....	97
4-8 Lithium Cells	97
4-9 Fuel Cells	98
4-10 Miniature Lamps and LEDs	99
4-11 Resistors	103
4-12 Switches	111
4-13 Wires and Cables	114
4-14 Fuses and Circuit Breakers	117
4-15 Other Components	122

Chapter 5 Multiple-Load Circuits 133

5-1	Subscripts	133
5-2	Power in Multiple-Load Circuits	133
5-3	Series Circuits	134
5-4	Maximum Power Transfer	141
5-5	Parallel Circuits	143
5-6	Conductance	150
5-7	Series-Parallel Circuits	152
5-8	Voltage Dividers and Regulators	156

Chapter 6 Complex-Circuit Analysis 173

6-1	Simultaneous Equations	173
6-2	Loop-Equations Technique	179
6-3	Node Voltage Technique	188
6-4	Superposition Theorem	193
6-5	Voltage Sources	197
6-6	Thevenin's Theorem	198
6-7	Current Source	204
6-8	Norton's Theorem	206
6-9	Comparison of Techniques	208

Chapter 7 Magnetism and Electromagnetism . . . 219

7-1	Magnetism and Magnets	219
7-2	Magnetic Fields, Flux, and Poles	219
7-3	Electromagnetism	223
7-4	Magnetic Materials	226
7-5	Magnetizing Magnetic Materials	227
7-6	Magnetomotive Force	228
7-7	Saturation	228
7-8	Demagnetizing	228
7-9	Residual Magnetism	229
7-10	Reluctance	229
7-11	Magnetic Shields	231
7-12	Induced Voltage	231
7-13	Magnetic Quantities and Units	234
7-14	Electromagnets	237
7-15	DC Motors	238
7-16	Solenoids	239
7-17	Relays	240
7-18	Hall-Effect Devices	241

Chapter 8 Alternating Current and Voltage. . . . 251

8-1	AC Terminology	251
8-2	Waveforms	251
8-3	Types of AC Waveforms	252
8-4	Quantifying Alternating Current	253
8-5	The Sine Wave	257
8-6	AC Generator	261
8-7	Advantages of Alternating Current	262
8-8	Three-Phase Alternating Current	263

Chapter 9 Power in AC Circuits. 281

9-1	Power in Resistive AC Circuits	281
9-2	Power in Out-of-Phase Circuits	282
9-3	True Power and Apparent Power	290
9-4	Power Factor	292
9-5	Power in Three-Phase Circuits	293

Chapter 10 Capacitance 303

10-1	Terminology	303
10-2	Basic Capacitor Action	303
10-3	Voltage Rating	305
10-4	Unit of Capacitance	305
10-5	Determining Capacitance	307
10-6	Types of Capacitors	309
10-7	Schematic Symbols	315
10-8	Capacitors in DC Circuits	315
10-9	Capacitors in AC Circuits	319
10-10	Capacitors in Series	323
10-11	Capacitors in Parallel	325
10-12	Detecting Faulty Capacitors	327
10-13	Undesired, or Stray, Capacitance	328
10-14	Capacitor Specifications	328
10-15	Uses of Capacitors	328

Chapter 11 Inductance 341

11-1	Characteristics of Inductance	341
11-2	Unit of Inductance—The Henry	344
11-3	Factors Determining Inductance	345
11-4	Types of Inductors	346
11-5	Ratings of Inductors	350
11-6	Inductors in DC Circuits	351
11-7	Ideal Inductors in AC Circuits	352
11-8	Real Inductors in AC Circuits	356
11-9	Inductors in Parallel	357
11-10	Inductors in Series	359
11-11	Time Constants for Inductors	360
11-12	Preventing Mutual Inductance	361
11-13	Undesired Inductance	361

Chapter 12 Transformers 373

12-1	Transformer Fundamentals	373
12-2	Efficiency of Transformers	379
12-3	Loaded and Unloaded Transformers	382
12-4	Transformer Cores	384
12-5	Types of Transformers	385
12-6	Impedance Matching	387
12-7	Transformer Ratings	389
12-8	Series and Parallel Windings	391
12-9	Off-Center-Tapped Windings	393
12-10	Three-Phase Transformers	394

Chapter 13 R, C, and L Circuits 409

13-1	Impedance	409
13-2	Adding Phasors	410
13-3	Solving RC Circuits	412
13-4	Solving RL Circuits	419
13-5	Solving RCL Circuits	422
13-6	Resonance	425
13-7	Filters	434

Chapter 14 Electric Motors 451

14-1	Motor Classifications	451
14-2	Motor Ratings	452
14-3	Motor Enclosures	459
14-4	Squirrel-Cage Induction Motors	460
14-5	Synchronous Motors	476
14-6	Other Types of Motors	477

Chapter 15 Instruments and Measurements 497

15-1	Digital Multimeter	497
15-2	Meter Movements	499
15-3	Analog Ammeters	502
15-4	Analog Voltmeters	506
15-5	Meter Loading	508
15-6	Analog Ohmmeters	510
15-7	Insulation Testers	511
15-8	Wheatstone Bridge	511
15-9	Wattmeters	512
15-10	Frequency Meters	515
15-11	Measuring Impedance	516
15-12	Measuring Inductance and Capacitance	517

Chapter 16 Residential Wiring Concepts 531

16-1	Electrical Codes	531
16-2	Power Distribution	531
16-3	Service Entrance	533
16-4	Cables and Conductors	535
16-5	240-V Branch Circuits	536
16-6	120-V Branch Circuits	537
16-7	Switched-Receptacle Outlet	541
16-8	Multiple Switching	541
16-9	Lighted-Handle Switches	544
16-10	Circuit Interrupters	545
16-11	Feeder Circuits	550
16-12	Low-Voltage Control Circuits	551
16-13	Electronic Control Circuits	556

Appendix A	Common Tools	569
Appendix B	Solder and the Soldering Process	576
Appendix C	Formulas and Conversions	581
Appendix D	Copper Wire Table	585
Appendix E	Resistivity of Metals and Alloys	586
Appendix F	Temperature Coefficients of Resistance	587
Appendix G	Trigonometric Functions	588
Appendix H	Capacitor Codes and Color Codes	589
Appendix I	The Oscilloscope	592
Appendix J	Basis of Cramer's Rule	603
Appendix K	Renewable Energy Sources and Technologies	604

Glossary of Terms and Symbols	606
---	-----

Index	612
-----------------	-----